

KADI SARVA VISHWAVIDYALAYA

B.E. Semester III EXAMINATION (April-2025)

Subject Code: CT304-N

Date: 29/04/2025

Time: 10:00am to 1:00pm

Subject Name: Digital Electronics

Total Marks: 70 Marks

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Use of scientific calculator is permitted.
4. Indicate clearly, the options you attempt along with its respective question number.
5. Use the last page of main supplementary for rough work.

Section-I

Q:1 Attempt Following.

- (A) (i) Convert $(725)_8$ (octal) to binary and hexadecimal. [5]
(ii) Convert $(101101.101)_2$ (binary) to decimal and octal.
- (B) (i) Convert $(2F3)_{16}$ (hexadecimal) to binary and decimal. [5]
(II) Convert $(187)_{10}$ (decimal) to binary and hexadecimal.
- (C) Why is the binary number system used in computers instead of the decimal system? What are the advantages of using the hexadecimal number system in computing? [5]

OR

- Q:1 (C) Perform $(1101)_2 - (1010)_2$ using 2's complement method. [5]
Multiply $(1011)_2 \times (110)_2$ in binary.

Q:2 Answer the following question.

- (A) How can a NAND gate be used to implement all basic logic gates (AND, OR, NOT) [5]
(B) Why is NAND logic preferred in digital circuit design for cost and efficiency reasons? [5]

OR

- Q:2 (A) Design the XOR function $F(A, B) = A \oplus B$ using a 2-variable K-map. [5]
(B) A Boolean function is given as: [5]
 $F(A, B, C) = \sum m(1, 2, 3, 5, 6)$
Use a 3-variable K-map to simplify the function.

Q:3 Answer the following question.

- (A) Design Full adder circuit and explain its working. [5]
(B) Design 3-bit Binary Parallel Adder and explain how does it work? [5]

OR

- Q:3 (A) What is a Magnitude Comparator, and where is it used? [5]
(B) Distinguish between: i) Master-Slave Flip Flop and Regular Flip Flop ii) Level Triggered Flip Flop and Edge Triggered flip flop? [5]

Section II

Q:4 Attempt following.

- (A) What are the basic components of a state machine? What is the difference between a Mealy and a Moore state machine? [5]
- (B) How does a synchronous state machine differ from an asynchronous state machine? [5]
- (C) Design 4-bit synchronous counters using D flip-flops and explain its working. [5]

OR

- Q:4 (C)** How can a J-K flip-flop be designed to work as a T flip-flop? [5]

Q:5 Answer the following question.

- (A) Distinguish between Programmable Logic Arrays (PLA) and Programmable Array Logic (PAL)? [5]
- (B) Write Short note of flash ADC. [5]

OR

- Q:5 (A)** What is the role of a Dual Slope A/D converter, and in which applications is it commonly used [5]
- (B)** Why do state machines require flip-flops for storing states? [5]

Q:6 Answer the following question.

- (A) Design a 4-bit shift register using D flip-flops that shifts data to the right on every clock pulse. [5]
- (B) What is the difference between an R-2R Ladder DAC and a Binary Weighted Resistor DAC? [5]

OR

- Q:6 (A)** Construct a D flip-flop using an S-R flip-flop and basic gates. [5]
- (B)** What is the main function of a Digital-to-Analog (D/A) converter, and where is it used? [5]