

KADI SARVA VISHWAVIDYALAYA

B.E. Semester III EXAMINATION (November-2024)

Subject Code: CT304-N
Date: 16/11/2024

Time: 12.30 to 3.30 PM

Subject Name: Digital Electronics
Total Marks: 70 Marks

Instructions:

1. All questions are compulsory.
2. Figures to the right indicate full marks.
3. Use of scientific calculator is permitted.
4. Indicate clearly, the options you attempt along with its respective question number.
5. Use the last page of main supplementary for rough work.

Section-I

Q:1 Attempt Following.

- (A) Explain D'Morgan's theorems in detail. [5]
- (B) Explain Excess-3 code in detail. [5]
- (C) Convert octal 623.77 to decimal, binary and hexadecimal. [5]

OR

Q:1 (C) Convert hexadecimal 2AC5.D to decimal and octal. [5]

Q:2 Answer the following question.

- (A) Write a short note about Full adder. [5]
- (B) Write a short note about Multiplexer. [5]

OR

- Q:2 (A) Write a short note about Magnitude comparator. [5]
- (B) Write a short note about decoder. [5]

Q:3 Answer the following question.

- (A) Write down a short note about 3 variable k-map using one example. [5]
- (B) Implement following Boolean function using only AND and NOT gates. [5]
(1) $F = x'z' + y'z' + yz' + xyz$

OR

- Q:3 (A) Perform binary subtraction with the following binary numbers using 1's and 2's complement. (a) 11010-1101. [5]
- (B) Explain NAND gate as universal gate. [5]

P.T.O

Section II

Q:4 Attempt following.

- (A) Explain difference between combinational circuits and sequential circuits.
- (B) Write down a short note about T flip flop.
- (C) Write down a short note about SR flip-flop.

[5]

[5]

[5]

OR

Q:4 (C) Write a short note about 4 bit binary ripple counter.

[5]

Q:5 Answer the following question.

- (A) Write down a short note about PLA.
- (B) Explain the Moore model of the state diagram.

[5]

[5]

OR

- Q:5 (A) What is ROM? Explain types of ROM memory.**
- (B) Write a short note about bidirectional shift register with neat diagram.**

[5]

[5]

Q:6 Answer the following question.

- (A) Write a short note about flash ADC.
- (B) Write a short note about R-2R ladder type DAC.

[5]

[5]

OR

- Q:6 (A) Enlist the Specifications of the Digital to Analog Converters (DAC).**
- (B) Write a short note on Dual slope type Analog to Digital Converters (ADC).**

[5]

[5]